

CHAPTER 22 REVIEW

Key Terms

22.1

- electric current
- conventional current
- battery
- photovoltaic cell
- electric circuit
- ampere
- resistance
- resistor
- potentiometer
- schematic
- parallel connection
- series connection

22.2

- kilowatt-hour

Summary

22.1 Current and Circuits

- Batteries, generators, and solar cells convert various forms of energy to electric energy.
- In an electric circuit, electric energy is transmitted from a device that produces electric energy to a resistor or other device that converts electric energy into the form needed.
- As a charge moves through resistors in a circuit, its potential energy is reduced. The energy released when the charge moves around the remainder of the circuit equals the work done to give the charge its initial potential energy.
- One ampere is one coulomb per second.
- Electric power is found by multiplying voltage by current.
- The resistance of a device is the ratio of the voltage across it divided by the current through it.

- In a device that obeys Ohm's law, the resistance remains constant as the voltage and current change.
- The current in a circuit can be varied by changing either the voltage or the resistance, or both.
- In a circuit diagram, conventional current is used. This is the direction in which a positive charge would move.

22.2 Using Electric Energy

- The thermal energy produced in a circuit from electric energy is equal to I^2Rt .
- In long-distance transmission, current is reduced without power being reduced by increasing the voltage.
- A kilowatt-hour, kWh, is an energy unit. It is equal to 3.6×10^6 J.

Reviewing Concepts

Section 22.1

1. Describe the energy conversions that occur in each of these devices.
 - a. incandescent lightbulb
 - b. clothes dryer
 - c. digital clock radio
2. Define the unit of electric current in terms of fundamental MKS units.
3. Which wire conducts electricity with the least resistance: one with a large cross-sectional diameter or one with a small cross-sectional diameter?
4. How many electrons flow past a point in a wire each second if the wire has a current of 1 A?

Section 22.2

5. Why do lightbulbs burn out more frequently just as they are switched on

6. A simple circuit consists of a battery, a resistor, and some connecting wires. Draw a circuit schematic of this simple circuit. Show the polarity of the battery and the direction of the conventional current.
7. A simple circuit consists of a resistor, a battery, and connecting wires.
 - a. How must an ammeter be connected in a circuit to correctly read the current?
 - b. How must a voltmeter be connected to a resistor in order to read the potential difference across it?
8. If a battery is short-circuited by a heavy copper wire being connected from one terminal to the other, the temperature of the copper wire rises.

Why does this happen?

9. Why does a wire become warmer as charges flow through it?
10. What electrical quantities must be kept small to transmit electric energy economically over long distances?

Applying Concepts

11. When a battery is connected to a complete circuit, charges flow in the circuit almost instantaneously. Explain.
12. Explain why a cow that touches an electric fence experiences a mild shock.
13. Why can birds perch on high-voltage lines without being injured?
14. Describe two ways to increase the current in a circuit.
15. You have two lightbulbs that work on a 120-V circuit. One is 50 W, the other is 100 W. Which bulb has a higher resistance? Explain.
16. If the voltage across a circuit is kept constant and the resistance is doubled, what effect does this have on the circuit's current?
17. What is the effect on the current in a circuit if both the voltage and the resistance are doubled? Explain.
18. Sue finds a device that looks like a resistor. When she connects it to a 1.5-V battery, only 45×10^{-6} A is measured, but when a 3.0-V battery is used, 25×10^{-3} A is measured. Does the device obey Ohm's law?
19. If the ammeter in **Figure 22-5** were moved to the bottom of the diagram, would the ammeter have the same reading? Explain.
20. Two wires can be placed across the terminals of a 6.0-V battery. One has a high resistance, and the other has a low resistance. Which wire will produce thermal energy at the faster rate? Why?
22. A current of 1.2 A is measured through a lightbulb when it is connected across a 120-V source. What power is dissipated by the bulb?
23. A lamp draws 0.50 A from a 120-V generator.
 - a. How much power is delivered?
 - b. How much energy does the lamp convert in 5.0 min?
24. A 12-V automobile battery is connected to an electric starter motor. The current through the motor is 210 A.
 - a. How many joules of energy does the battery deliver to the motor each second?
 - b. What power, in watts, does the motor use?
25. A 4000-W clothes dryer is connected to a 220-V circuit. How much current does the dryer draw?
26. A flashlight bulb is connected across a 3.0-V potential difference. The current through the lamp is 1.5 A.
 - a. What is the power rating of the lamp?
 - b. How much electric energy does the lamp convert in 11 min?
27. A resistance of 60Ω has a current of 0.40 A through it when it is connected to the terminals of a battery. What is the voltage of the battery?
28. What voltage is applied to a $4.0\text{-}\Omega$ resistor if the current is 1.5 A?
29. What voltage is placed across a motor of $15\text{-}\Omega$ operating resistance if there is 8.0 A of current?
30. A voltage of 75 V is placed across a $15\text{-}\Omega$ resistor. What is the current through the resistor?
31. A $20.0\text{-}\Omega$ resistor is connected to a 30.0-V battery. What is the current through the resistor?
32. A 12-V battery is connected to a device and 24 mA of current is measured. If the device obeys Ohm's law, how much current is present when a 24-V battery is used?
33. A person with dry skin has a resistance from one arm to the other of about $1 \times 10^5 \Omega$. When skin is wet, resistance drops to about $1.5 \times 10^3 \Omega$. (refer to **Table 22-1**).
 - a. What is the minimum voltage placed across the arms that would produce a current that could be felt by a person with dry skin?
 - b. What effect would the same voltage have if the person had wet skin?

Problems

Section 22.1

LEVEL 1

21. The current through a toaster connected to a 120-V source is 8.0 A. What power is dissipated by the toaster?